

**At least one window is open**

Push button 1 open


Push button 2 closed

12 v supply



A/C controller  
(A/C stops  
because relay  
is closed)

12 v supply

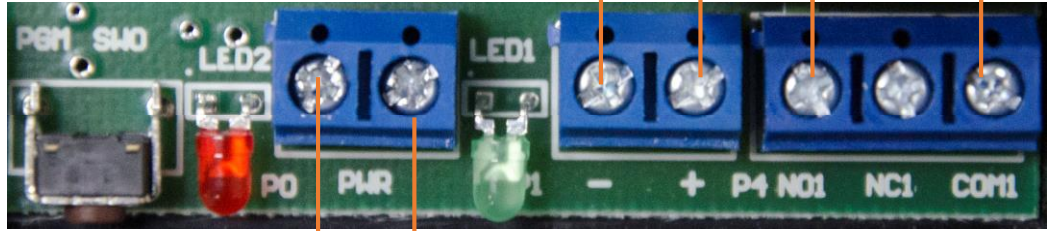

Mimo relay - Normally open

# Closed windows

Push button 1 closed


Push button 2 closed

12 v supply



A/C controller  
(A/C on because  
relay is open)

12 v supply

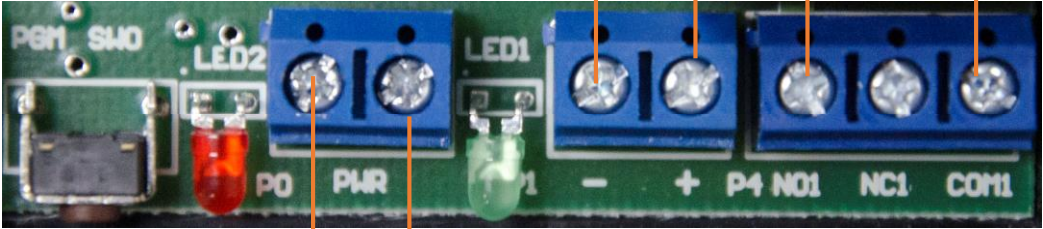

Mimo relay - Normally open